



## Sheet (4) MOSFET

### Problem (1)

Indicate whether each of the following statements is true or false

1. The current direction in NMOS transistor is from source to drain.
2. MOSFET transistor is a device in which lateral current is controlled by vertical electric field.
3. Channel in NMOS is created due to capacitance effect of the transistor gate.
4. MOSFET can be used as a voltage-controlled-resistor (VCR) at small  $V_{DS}$ .
5. For ideal MOSFET, the resistance between drain and source is infinite at triode region.

### Problem (2)

For the circuits shown on Figure 1 find the value of  $R_S$  and  $R_D$ . If

$$I_D = 0.4 \text{ mA and } V_D = +0.5 \text{ V.}$$

$$V_t = 0.7 \text{ V, } \mu_n C_{ox} = 100 \mu\text{A/V}^2, L = 1 \mu\text{m, and } W = 32 \mu\text{m.}$$

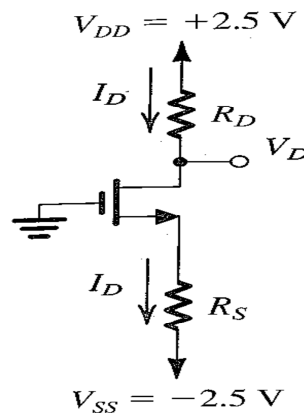


Fig 1

### **Problem (3)**

For the circuits shown on Figure 1 find the value of R. If

$$I_D \text{ of } 80 \mu\text{A}, V_t = 0.6 \text{ V}, \mu_n C_{ox} = 200 \mu\text{A/V}^2.$$

$$L = 0.8 \mu\text{m}, \text{ and } W = 4 \mu\text{m}$$

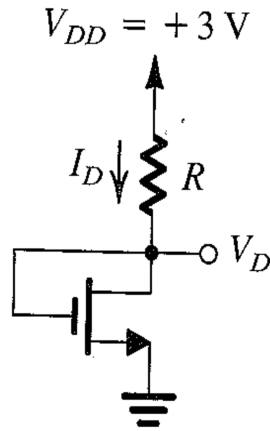


Fig 2

### **Problem (4)**

For the circuits shown on Figure 3 find all the node voltages and branch currents.

$$\text{Let } V_t = 1 \text{ V and } k'_n(W/L) = 1 \text{ mA/V}^2.$$

What happen if?

a-  $R_D = 14$ .

b-  $R_S = 10$ .

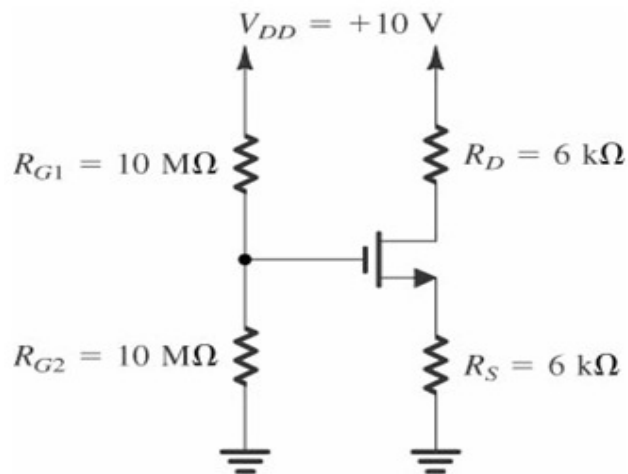


Fig 3

**Problem (5)**

For the circuits shown on Figure 4 find the value of  $R_{G1}$  and  $R_{G2}$  to make the transistor in sat. If

$$V_t = -1 \text{ V and } k_p'(W/L) = 1 \text{ mA/V}^2.$$

Solve it with the graphical solution, if we know  $R_{G1}$  and  $R_{G2}$ .

What is the largest value of  $R_D$  to make the transistor in sat.

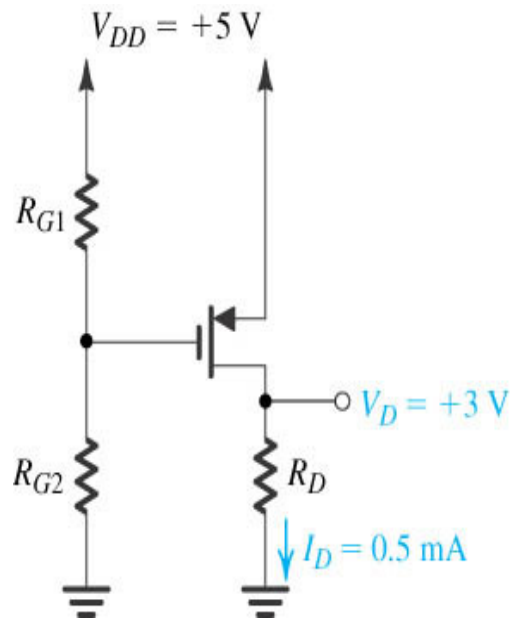


Fig 4